

Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eecs303/>

Teacher: Robert Dick
Office: L477 Tech
Email: dickrp@northwestern.edu
Phone: 847-467-2298



NORTHWESTERN
UNIVERSITY

Outline

1. Sequential elements
2. Finite state machine design
3. Homework

Section outline

1. Sequential elements

Introduction

Reset/set latches

Clocking conventions

D flip-flop


Flip-flop introduction

- Stores, and outputs, a value
- Puts a special clock signal in charge of timing
- Allows output to change in response to clock transition
- More on this later
 - Timing and sequential circuits

Introduction to sequential elements


- Feedback and memory
- Memory
- Latches

Feedback and memory

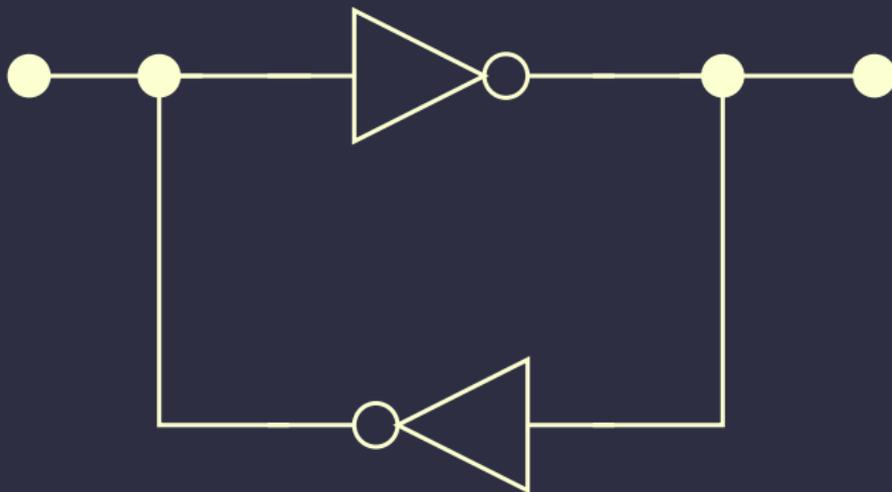


- Feedback is the root of memory
- Can compose a simple loop from NOT gates

Feedback and memory

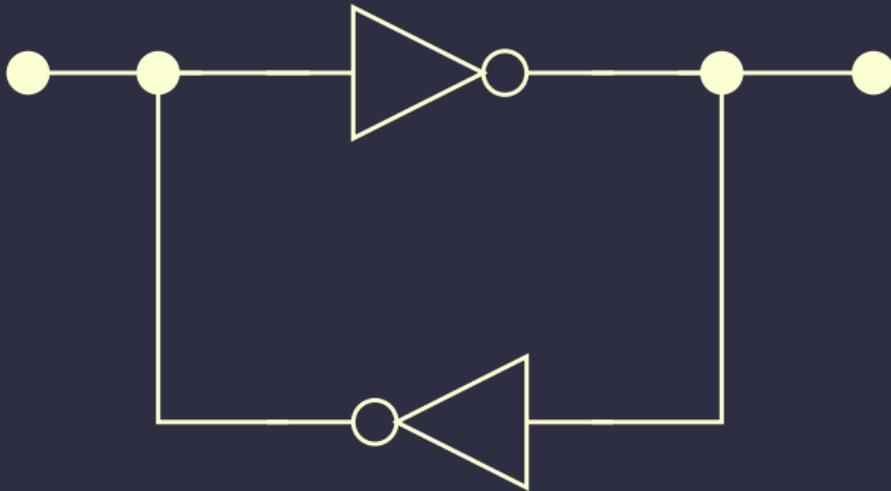

- Feedback is the root of memory
- Can compose a simple loop from NOT gates
- However, there is no way to switch the value

TG and NOT-based memory

 

- Can break feedback path to load new value
- However, potential for timing problems

Section outline

1. Sequential elements



Introduction

Reset/set latches


Clocking conventions

D flip-flop

Reset/set latch

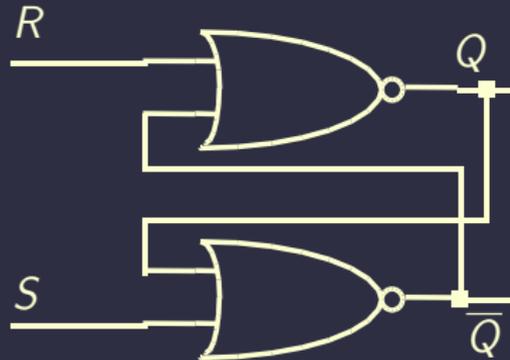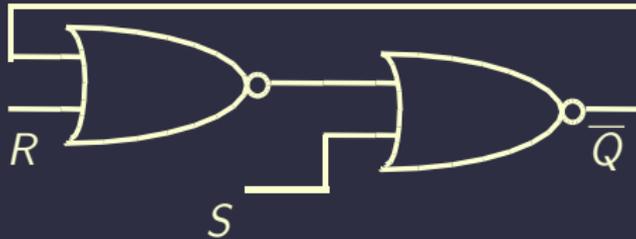


Reset/set timing

 


RS latch state diagram

output = $Q \bar{Q}$
input = $R S$

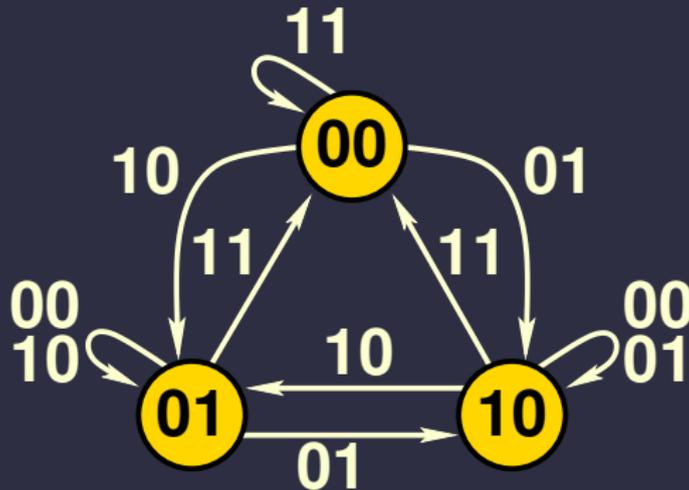


Clocking terms

 


- Clock – Rising edge, falling edge, high level, low level, period
- Setup time: Minimum time before clocking event by which input must be stable (T_{SU})
- Hold time: Minimum time after clocking event for which input must remain stable (T_H)
- Window: From setup time to hold time

Gated RS latch

 

Gated RS latch

 

Memory element properties

Type	Inputs sampled	Outputs valid
Unclocked latch	Always	LFT
Level-sensitive latch	Clock high	LFT
Edge-triggered flip-flop	(T_{SU} to T_H) around falling clock edge Clock low-to-high transition (T_{SU} to T_H) around rising clock edge	Delay from rising edge

Section outline

1. Sequential elements

Introduction

Reset/set latches

Clocking conventions

D flip-flop

Clocking conventions

Active-high transparent



Active-low transparent




Positive (rising) edge



Negative (falling) edge



 Timing for edge and level-sensitive latches




Latch timing specifications

- Minimum clock width, T_W
 - Usually period / 2
- Low to high propagation delay, P_{LH}
- High to low propagation delay, P_{HL}
- Worst-case and typical

Latch timing specifications

 Example, negative (falling) edge-triggered flip-flop timing diagram




FF timing specifications

- Minimum clock width, T_W
 - Usually period / 2
- Low to high propagation delay, P_{LH}
- High to low propagation delay, P_{HL}

FF timing specifications

 
Example, positive (rising) edge-triggered flip-flop timing diagram



RS latch states

S	R	Q^+	\overline{Q}^+	Notes
0	0	Q	\overline{Q}	
0	1	0	1	
1	0	1	0	
1	1	1	1	unstable

JK latch

 


Use output feedback to ensure that $RS \neq 11$

$$Q^+ = Q \bar{K} + \bar{Q} J$$

JK latch

J	K	Q	Q^+	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	1	toggle
1	1	1	0	

JK race

 

Section outline

1. Sequential elements

Introduction

Reset/set latches


Clocking conventions

D flip-flop


Falling edge-triggered D flip-flop

- Use two stages of latches
- When clock is high
 - First stage samples input w.o. changing second stage
 - Second stage holds value
- When clock goes low
 - First stage holds value and sets or resets second stage
 - Second stage transmits first stage
- $Q^+ = D$
- One of the most commonly used flip-flops

Falling edge-triggered D flip-flop

 


Falling edge-triggered D flip-flop

 


Clock switching

Inputs sampled on falling edge, outputs change after falling edge

Falling edge-triggered D flip-flop

 

Edge triggered timing

 

RS clocked latch

- Storage element in narrow width clocked systems
- Dangerous
- Fundamental building block of many flip-flop types

JK flip-flop

- Versatile building block
- Building block for D and T flip-flops
- Has two inputs resulting in increased wiring complexity
- Don't use master/slave JK flip-flops
 - Ones or zeros catching
- Edge-triggered varieties exist

D flip-flop

- Minimizes input wiring
- Simple to use
- Common choice for basic memory elements in sequential circuits

Toggle (T) flip-flops

- State changes each clock tick
- Useful for building counters
- Can be implemented with other flip-flops
 - JK with inputs high
 - D with XOR feedback

Asynchronous inputs

- How can a circuit with numerous distributed edge-triggered flip-flops be put into a known state
- Could devise some sequence of input events to bring the machine into a known state
 - Complicated
 - Slow
 - Not necessarily possible, given trap states
- Can also use sequential elements with additional asynchronous reset and/or set inputs

Latch and flip-flop equations

RS

$$Q^+ = S + \bar{R} Q$$

D

$$Q^+ = D$$

Latch and flip-flop equations

JK

$$Q^+ = J \bar{Q} + \bar{K} Q$$

T

$$Q^+ = T \oplus Q$$

Outline

1. Sequential elements
2. Finite state machine design
3. Homework

Section outline

2. Finite state machine design

Regular expressions

Nondeterministic finite state automata

Deterministic finite state automata

Finite state machines

State equations and minimization

Sequential FSM design example

- We'll walk through the design of an example finite state machine (FSM)
- Some of the stages will be covered in more detail in later lectures
- I want you to have a high-level understanding of our overall goal before covering every detail of FSM synthesis

Regular expressions

- Naturally express control
- However, no simple direct HW implementation
- We want to get to sequential logic
- Need to go through other stages first

Regular expressions

Can be expressed with regular expressions, examples

- Accept the empty string, ϵ
- Accept nothing, \emptyset
- Accept 0 or 11, $(0 + 11)$
- Accept anything starting with 1 and one or more 0 and ending with 0 or 10, $10^+(0 + 10)$
- Accept anything starting with zero or more 0010 or 1 and ending with 1, $(0010 + 1)^*1$

Section outline

2. Finite state machine design

Regular expressions

Nondeterministic finite state automata

Deterministic finite state automata

Finite state machines

State equations and minimization

Nondeterministic finite state automata (NFA)


- State graph
- Multiple states can be active at the same time
- Some states ACCEPT
- The automata accepts if any accepting states are active

NFA

$$(101 + 01 + \epsilon)(11)^+$$


NFA

$$(101 + 01 + \epsilon)(11)^+$$

 


NFA

$$(101 + 01 + \epsilon)(11)^+$$

 


NFA

$$(101 + 01 + \epsilon)(11)^+$$

 


NFA

$$(101 + 01 + \epsilon)(11)^+$$

 

NFA


$$(101 + 01 + \epsilon)(11)^+$$

 

0 1


NFA

$$(101 + 01 + \epsilon)(11)^+$$

 

NFA


$$(101 + 01 + \epsilon)(11)^+$$

 

0 1 1

NFA


$$(101 + 01 + \epsilon)(11)^+$$

 

0 1 1 1

NFA

$$(101 + 01 + \epsilon)(11)^+$$

 

0 1 1 1

Section outline

2. Finite state machine design

Regular expressions

Nondeterministic finite state automata

Deterministic finite state automata

Finite state machines

State equations and minimization

Deterministic finite state automata (DFA)

- NFAs require multiple states to be simultaneously active
- Can't represent this with conventional logic state variables
- Need to convert to deterministic representation

DFA

$$(101 + 01 + \epsilon)(11)^+$$


DFA

$$(101 + 01 + \epsilon)(11)^+$$




DFA


$$(101 + 01 + \epsilon)(11)^+$$

 


DFA

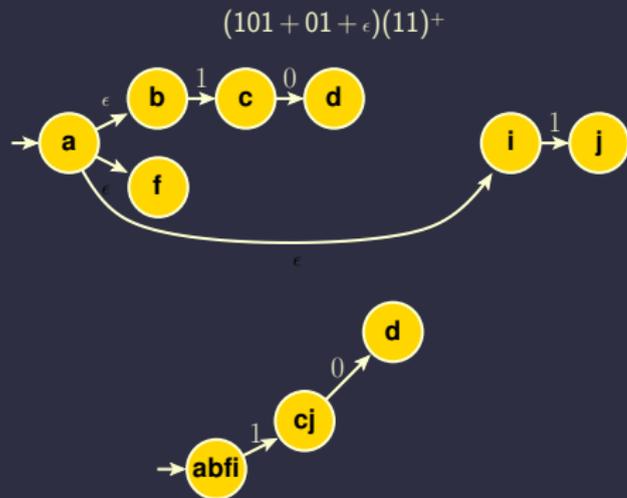


DFA

 


DFA

 


DFA

 


DFA

 

DFA

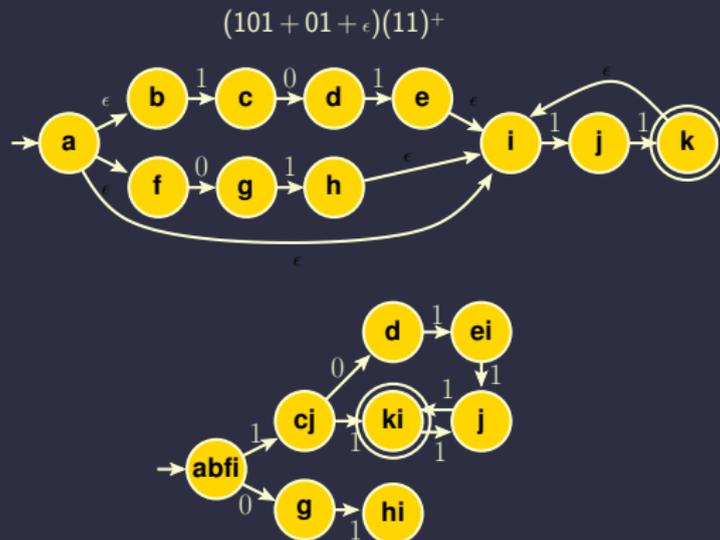


DFA

 


DFA to more explicit FSM

$$(101 + 01 + \epsilon)(11)^+$$

 


DFA to more explicit FSM

$$(101 + 01 + \epsilon)(11)^+$$

 


DFA to more explicit FSM

$$(101 + 01 + \epsilon)(11)^+$$

 

DFA to more explicit FSM

$$(101 + 01 + \epsilon)(11)^+$$

 

Section outline

2. Finite state machine design

Regular expressions

Nondeterministic finite state automata

Deterministic finite state automata


Finite state machines

State equations and minimization


DFA to FSM

- DFA may only accept or reject
- Simple to convert Moore FSM
- Add explicit output values to states


Moore block diagram

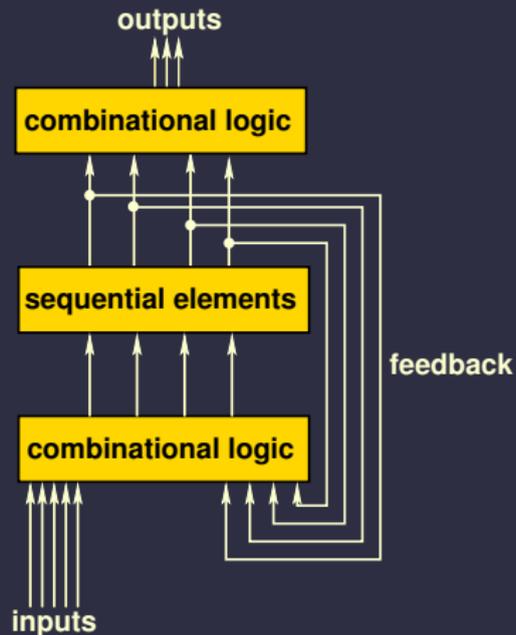

Mealy block diagram

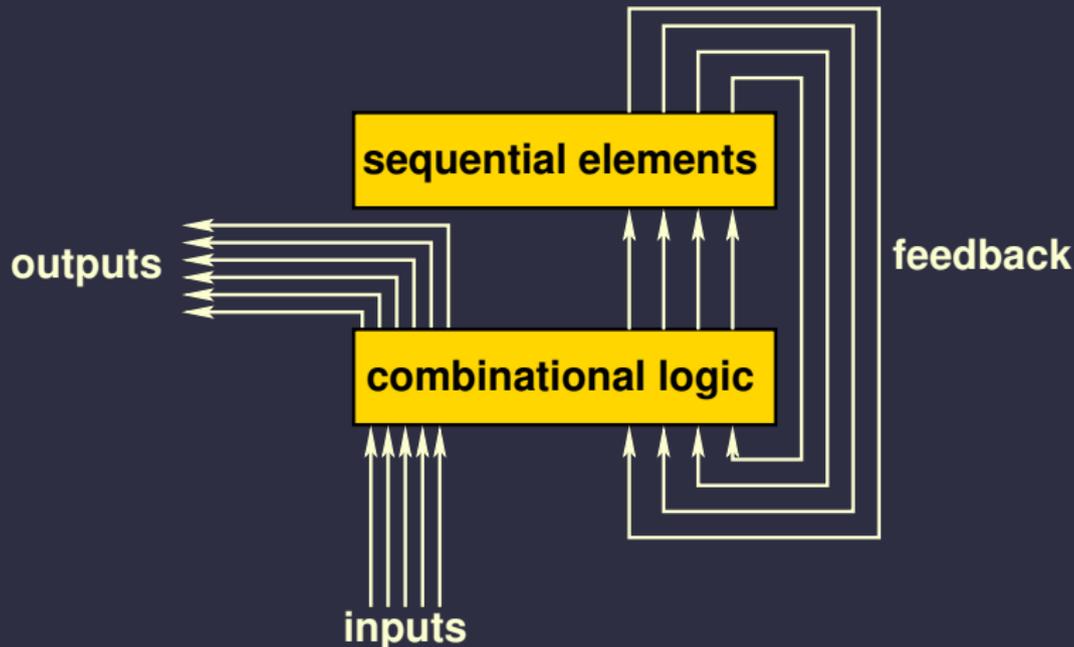

Moore FSMs

 

Section outline

2. Finite state machine design

Regular expressions

Nondeterministic finite state automata

Deterministic finite state automata

Finite state machines

State equations and minimization

Introduction to state reduction

s	s ⁺		Q
	0	1	
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1

Introduction to state reduction

s	s ⁺		Q
	0	1	
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1

Introduction to state reduction

s	s^+		q
	0	1	
AC	AC	B	0
B	AC	B	0
D	AC	AC	1

Introduction to state reduction

s	s^+		q
	0	1	
AC	AC	B	0
B	AC	B	0
D	AC	AC	1

Introduction to state reduction

s	s^+		q
	0	1	
AC	AC	B	0
B	AC	B	0
D	AC	AC	1

State assignment

s	s^+		q
	0	1	
ABC	ABC	ABC	0
D	ABC	ABC	1

State assignment

s	s ⁺		q
	0	1	
ABC	ABC	ABC	0
D	ABC	ABC	1

Only two adjacent states, state assignment is trivial

State assignment

s	s^+		q
	0	1	
ABC	ABC	ABC	0
D	ABC	ABC	1

Only two adjacent states, state assignment is trivial
However, good to consider output, q

State variable functions

s	s ⁺		q
	0	1	
0	0	0	0
1	0	0	1

State variable functions

	s^+		
s	0	1	q
0	0	0	0
1	0	0	1

$s^+(s) = 0$


State variable functions

s	s^+		q
	0	1	
0	0	0	0
1	0	0	1

$$s^+(s) = 0$$

$$q(s) = s$$



Mealy FSMs

 


Mealy tabular form

s	s ⁺ /q	
	0	1
A	D/0	B/X
B	C/1	B/0
C	A/0	B/1
D	C/1	C/0


Mealy to Moore conversion

  

State variable combinational synthesis

 


State variable combinational synthesis

 

- Separate sequential and combinational portions of circuit

State variable combinational synthesis

 

- Separate sequential and combinational portions of circuit
- Conduct standard logic synthesis

FSM design summary

- Specify requirements in natural form – regular expression or NFA
- Converting from NFA to DFA is straightforward
- Converting from DFA to FSM is straightforward
- Minimize the number of states using compatible states, class sets, and binate covering
- Assign values to states to minimize logic complexity
- Allow only adjacent or path transitions for asynchronous machines
- Optimize implementation of state and output functions

Outline

1. Sequential elements
2. Finite state machine design
3. Homework

Recommended reading

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, third edition, 2004
- Chapter 7
- Chapter 6

Video controller repair lab

- Design a finite state machine based on an English problem specification
- The design problem isn't very difficult
- Going from a real-world problem to a formal representation may be difficult
- Be careful not to use too many state variables!!!
 - Could easily turn it from a 6-hour lab to a 12-hour lab

Next lecture

- More detail and examples on FSM design and optimization